

Digital Logic Circuits 'Sequential Logic Design' ELEC2200 Summer 2009

David J. Broderick
brodedj@auburn.edu
<http://www.auburn.edu/~brodedj>
Office: Broun 360



Example

- Looking up circuits in a book only useful to a point
- Example: Design a 3 bit gray code counter with an active low, synchronous reset. Transitions should occur on the rising edge.
- Not a common circuit, we'll have to design ourselves
- What steps do we need to take?



Basic Steps

- 1) Describe the state machine based on the design spec
 - 3 different ways
- 2) Choose flip-flops
- 3) Create circuit excitation table
- 4) Construct K-maps for:
 - flip-flop inputs
 - primary outputs
- 5) Obtain minimized SOP equations
- 6) Draw logic diagram
- 7) Simulate to verify design & debug as needed
- 8) Perform circuit analysis & logic optimization




State Machine

- A state diagram describes the behavior of a finite state machine (FSM). Can also use:
 - A state table
 - Truth table format
- A FSM is a model of a device that can be described by:
 - A finite number of states
 - Stimuli and related transitions
 - Outputs



State Diagram

 
- In this case output is equivalent to state
- FSM is initialized to 000_2 state
- If $R=1$, move to next count
- If $R=0$, reset to zero
- Active low reset
- Design calls for rising edge triggered flip-flops



State Table

- Contains the same information in a different format
- Current state and input as column, row headings
- Next state as cell in table


| State\R | 0 | 1 |
|---------|-----|-----|
| 000 | 000 | 001 |
| 001 | 000 | 011 |
| 011 | 000 | 010 |
| 010 | 000 | 110 |
| 110 | 000 | 111 |
| 111 | 000 | 101 |
| 101 | 000 | 100 |
| 100 | 000 | 000 |

 


Truth Table

- Contains the same information in a different format
- If it's not in the table, we “don't care”

| Input R | Curr. State | | | Next State | | |
|---------|-------------|---|---|------------|---|---|
| R | 2 | 1 | 0 | 2 | 1 | 0 |
| 0 | x | x | x | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 |

 

Basic Steps

1) Describe the state machine based on the design spec
- 3 different ways 

2) Choose flip-flops

3) Create circuit excitation table

4) Construct K-maps for:

- flip-flop inputs
- primary outputs

5) Obtain minimized SOP equations

6) Draw logic diagram

7) Simulate to verify design & debug as needed

8) Perform circuit analysis & logic optimization




Choosing Flip-Flops

- Any type will work
- Some will result in a simpler, smaller circuit
- For sequential design typically JK and D flip-flops
- T flip-flops typically used for counter designs
- Let's mix it up for our example and use all types



Choosing Flip-Flops

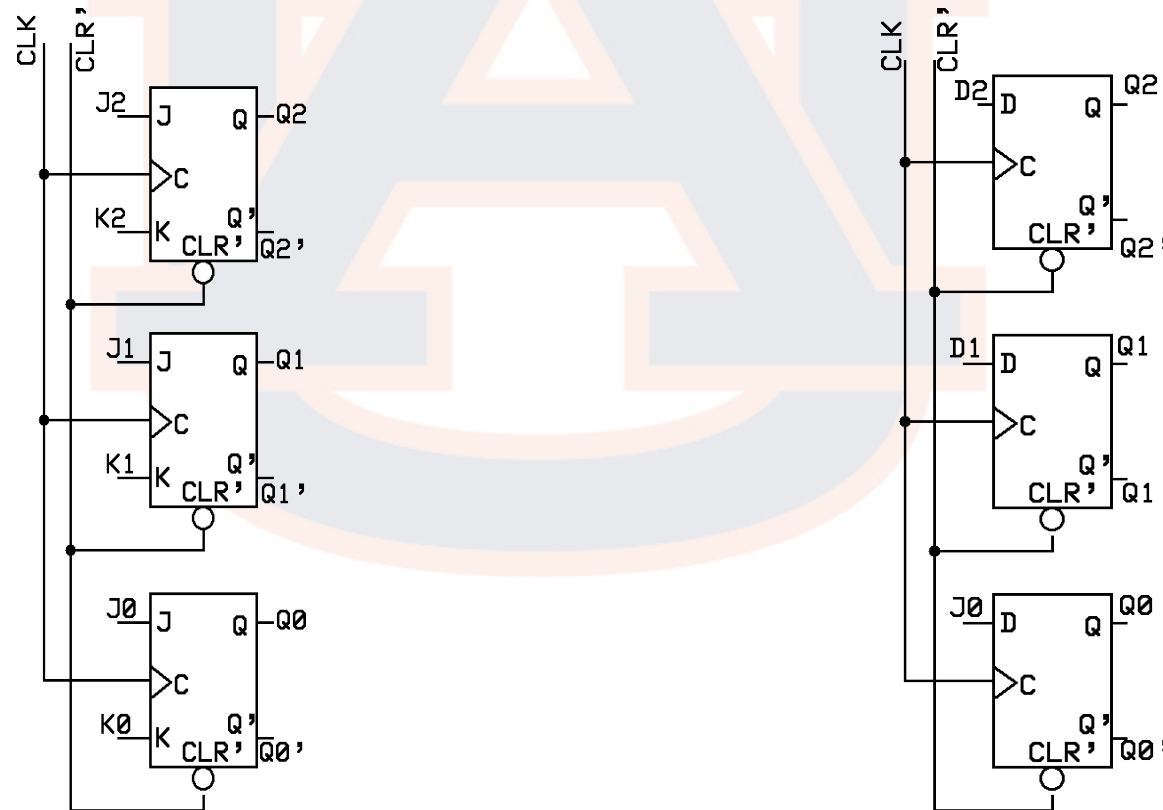- Each state is represented by a binary value
- Binary value must have enough bits to represent all of the states
- Here, 8 states \rightarrow 3 bits



Basic Steps

- 1) Describe the state machine based on the design spec
 - 3 different ways
- 2) Choose flip-flops
- 3) Create circuit excitation table**
- 4) Construct K-maps for:
 - flip-flop inputs
 - primary outputs
- 5) Obtain minimized SOP equations
- 6) Draw logic diagram
- 7) Simulate to verify design & debug as needed
- 8) Perform circuit analysis & logic optimization




Circuit Excitation Table

- Excitation table contains information to answer: “What inputs are needed to move a flip-flop from the current state to the next state?”
- Build table by:
 - Copying the state machine truth table
 - Adding columns for each flip-flop input



Circuit Excitation Table

- For JK flip-flops:

 


| Input | Curr. State | | | Next State | | | Q2 | | Q1 | | Q0 | |
|-------|-------------|---|---|------------|---|---|----|---|----|---|----|---|
| | 2 | 1 | 0 | 2 | 1 | 0 | J | K | J | K | J | K |
| 0 | x | x | x | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | x | 0 | x | 1 | x |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | x | 1 | x | x | 0 |
| 1 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | x | x | 0 | x | 1 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | x | x | 0 | 0 | x |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 | x | 0 | x | 0 | 1 | x |
| 1 | 1 | 1 | 1 | 1 | 0 | 1 | x | 0 | x | 1 | x | 0 |
| 1 | 1 | 0 | 1 | 1 | 0 | 0 | x | 0 | 0 | x | x | 1 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | x | 1 | 0 | x | 0 | x |



Circuit Excitation Table

- For D flip-flops:

 

| Input | Curr. State | Next State | Q2 | Q1 | Q0 | | | | |
|----------|-------------|------------|----------|----------|----------|----------|----------|----------|----------|
| R | 2 | 1 | 0 | 2 | 1 | 0 | D | D | D |
| 0 | x | x | x | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |



Basic Steps

- 1) Describe the state machine based on the design spec
 - 3 different ways
- 2) Choose flip-flops
- 3) Create circuit excitation table
- 4) **Construct K-maps for:**
 - **flip-flop inputs**
 - **primary outputs**
- 5) **Obtain minimized SOP equations**
- 6) Draw logic diagram
- 7) Simulate to verify design & debug as needed
- 8) Perform circuit analysis & logic optimization



Create K-Maps

- Each flip-flop input is driven by a combinational circuit
- Inputs to each circuit are:
 - the current state as indicated by the current flip-flop outputs
 - External inputs (reset in this case) used to control which transition occurs



JK K-Maps

| R,Q2\ Q1,Q0 | J2 | | | |
|----------------|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | 0 | 0 | 0 | 0 |
| 01 | 0 | 0 | 0 | 0 |
| 11 | x | x | x | x |
| 10 | 0 | 0 | 0 | 1 |

| R,Q2\ Q1,Q0 | J1 | | | |
|----------------|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | 0 | 0 | 0 | 0 |
| 01 | 0 | 0 | 0 | 0 |
| 11 | 0 | 0 | x | x |
| 10 | 0 | 1 | x | x |

| R,Q2\ Q1,Q0 | J0 | | | |
|----------------|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | 0 | 0 | 0 | 0 |
| 01 | 0 | 0 | 0 | 0 |
| 11 | 0 | x | x | 1 |
| 10 | 1 | x | x | 0 |

| R,Q2\ Q1,Q0 | K2 | | | |
|----------------|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | 1 | 1 | 1 | 1 |
| 01 | 1 | 1 | 1 | 1 |
| 11 | 1 | 0 | 0 | 0 |
| 10 | x | x | x | x |

| R,Q2\ Q1,Q0 | K1 | | | |
|----------------|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | 1 | 1 | 1 | 1 |
| 01 | 1 | 1 | 1 | 1 |
| 11 | x | x | 1 | 0 |
| 10 | x | x | 0 | 0 |

| R,Q2\ Q1,Q0 | K0 | | | |
|----------------|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | 1 | 1 | 1 | 1 |
| 01 | 1 | 1 | 1 | 1 |
| 11 | x | 1 | 0 | x |
| 10 | x | 0 | 1 | x |

$$J2 = R \cdot Q1 \cdot \overline{Q0}$$

$$K2 = \overline{R} + Q1 \cdot Q0$$

$$J1 = R \cdot \overline{Q2} \cdot Q0$$

$$K1 = \overline{R} + Q2 \cdot Q0$$

$$J0 = R \cdot \overline{Q2} \cdot Q1 + R \cdot Q2 \cdot Q1$$

$$K0 = \overline{R} + Q2 \cdot Q1 + Q2 \cdot Q1$$



D K-Maps

| R,Q2\ Q1,Q0 | D2 | | | | R,Q2\ Q1,Q0 | D1 | | | | R,Q2\ Q1,Q0 | D0 | | | |
|----------------|----|----|----|----|----------------|----|----|----|----|----------------|----|----|----|----|
| | 00 | 01 | 11 | 10 | | 00 | 01 | 11 | 10 | | 00 | 01 | 11 | 10 |
| 00 | 0 | 0 | 0 | 0 | 00 | 0 | 0 | 0 | 0 | 00 | 0 | 0 | 0 | 0 |
| 01 | 0 | 0 | 0 | 0 | 01 | 0 | 0 | 0 | 0 | 01 | 0 | 0 | 0 | 0 |
| 11 | 0 | 1 | 1 | 1 | 11 | 0 | 0 | 0 | 1 | 11 | 0 | 0 | 1 | 1 |
| 10 | 0 | 0 | 0 | 1 | 10 | 0 | 1 | 1 | 1 | 10 | 1 | 1 | 0 | 0 |

$$D2 = R \cdot Q2 \cdot Q0 + R \cdot Q2 \cdot Q1 + R \cdot Q1 \cdot \overline{Q0}$$

$$D0 = R \cdot \overline{Q2} \cdot \overline{Q1} + R \cdot Q2 \cdot Q1$$

$$D1 = R \cdot \overline{Q2} \cdot Q0 + R \cdot \overline{Q2} \cdot Q1 + R \cdot Q1 \cdot \overline{Q0}$$




Basic Steps


- 1) Describe the state machine based on the design spec
 - 3 different ways
- 2) Choose flip-flops
- 3) Create circuit excitation table
- 4) Construct K-maps for:
 - flip-flop inputs
 - primary outputs
- 5) Obtain minimized SOP equations
- 6) Draw logic diagram**
- 7) Simulate to verify design & debug as needed
- 8) Perform circuit analysis & logic optimization



Circuit Diagram – See Handout

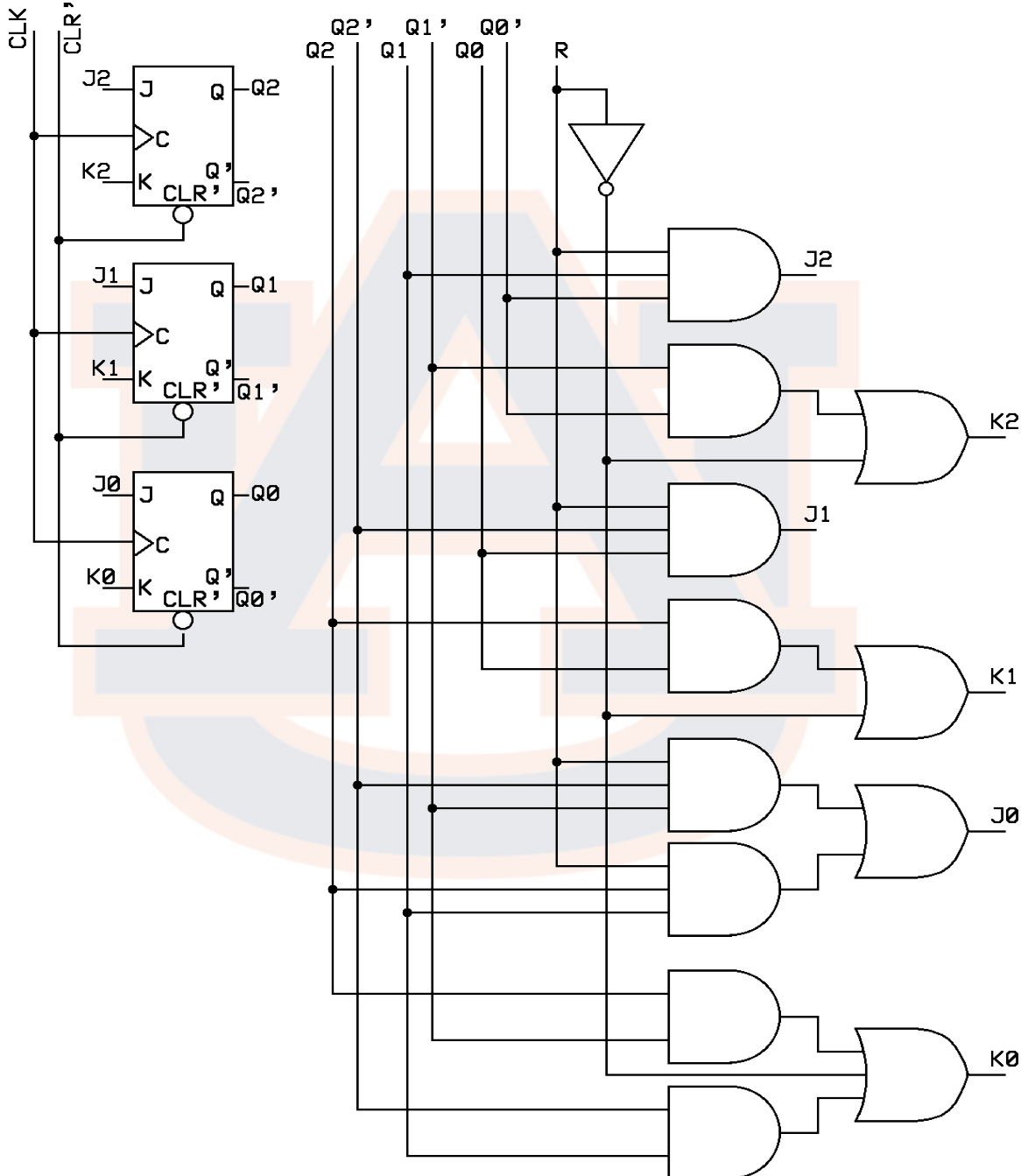

Circuit Diagram – See Handout

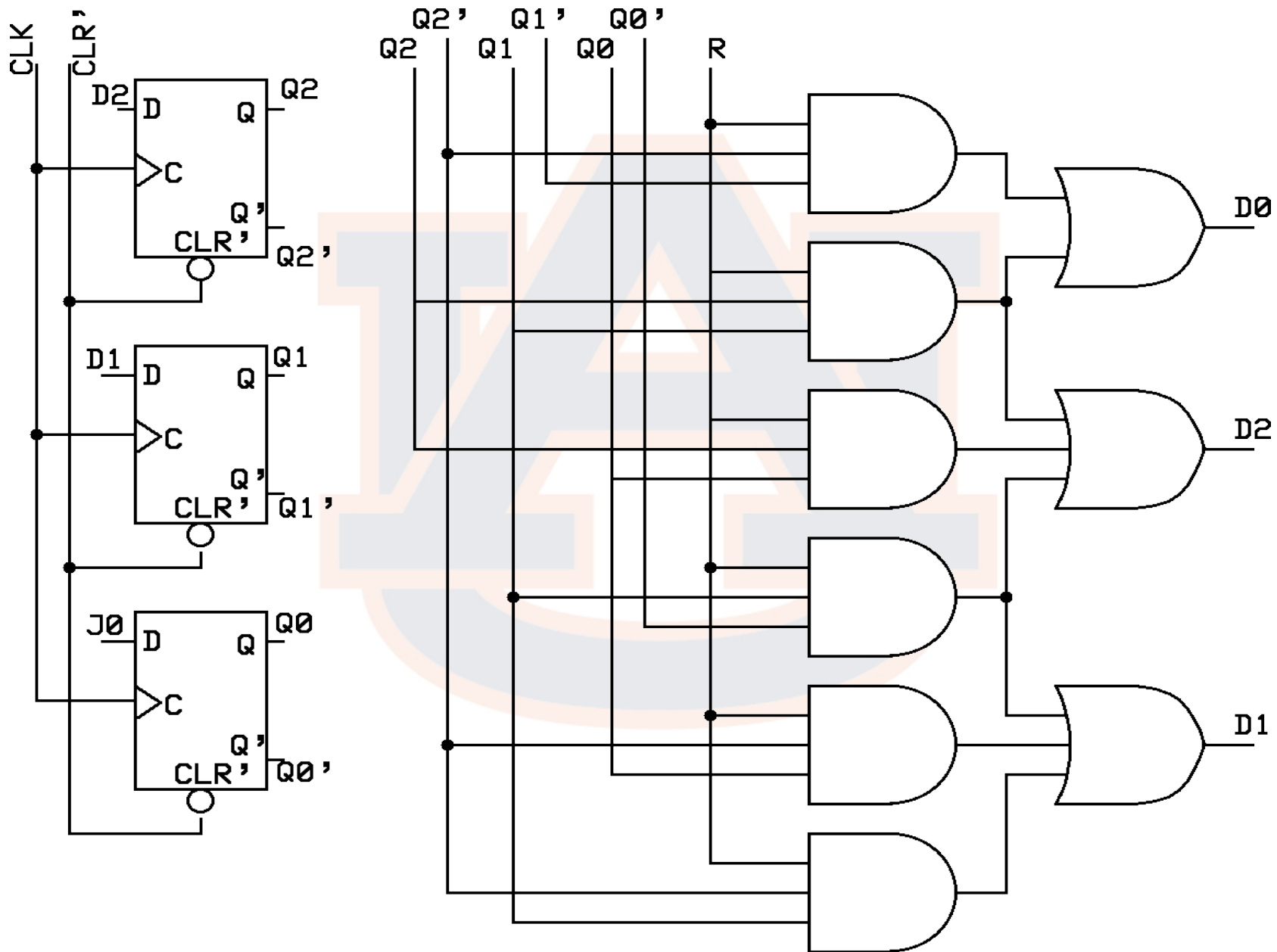

Basic Steps

- 1) Describe the state machine based on the design spec
 - 3 different ways
- 2) Choose flip-flops
- 3) Create circuit excitation table
- 4) Construct K-maps for:
 - flip-flop inputs
 - primary outputs
- 5) Obtain minimized SOP equations
- 6) Draw logic diagram
- 7) Simulate to verify design & debug as needed**
- 8) Perform circuit analysis & logic optimization



Simulation

- AUSIM can simulate sequential circuits too
- Flip-flops in AUSIM:
 - dff: FF1 in: CLK D out: Q QN ; (D flip-flop)
 - jkff: FF2 in: CLK J K out: Q QN ; (JK flip-flop)
 - srff: FF3 in: CLK S R out: Q QN ; (SR flip-flop)
- Q's and QN's become input to the combinational circuit designed above in addition to R
- Input to this circuit is the Clock(C) and the Reset (R)
- Output of this circuit is Q2,Q1,Q0



Simulation

DFF Circuit

```
ckt: 3bitgray in: c R out: Q2 Q1 Q0 ;  
dff: DFF2 in: c d2 out: Q2 Q2N ;  
dff: DFF1 in: c d1 out: Q1 Q1N ;  
dff: DFF0 in: c d0 out: Q0 Q0N ;  
and: G1 in: R Q2 Q0 out: G1 ;  
and: G2 in: R Q2 Q1 out: G2 ;  
and: G3 in: R Q1 Q0N out: G3 ;  
or: G4 in: G1 G2 G3 out: d2 ;  
and: G5 in: R Q2N Q0 out: G5 ;  
and: G6 in: R Q2N Q1 out: G6 ;  
or: G7 in: G3 G5 G6 out: d1 ;  
and: G8 in: R Q2N Q1N out: G8 ;  
or: G9 in: G2 G8 out: d0 ;
```


JKFF Circuit

```
ckt: 3bitgray in: c R out: Q2 Q1 Q0 ;  
jkff: JKFF2 in: c J2 K2 out: Q2 Q2N ;  
jkff: JKFF1 in: c J1 K1 out: Q1 Q1N ;  
jkff: JKFF0 in: c J0 K0 out: Q0 Q0N ;  
not: G0 in: R out: RN ;  
and: G1 in: R Q1 Q0N out: J2 ;  
and: G2 in: Q1N Q0N out: G2 ;  
or: G3 in: RN G2 out: K2 ;  
and: G4 in: R Q2N Q0 out: J1 ;  
and: G5 in: Q2 Q0 out: G5 ;  
or: G6 in: RN G5 out: K1 ;  
and: G7 in: R Q2N Q1N out: G7 ;  
and: G8 in: R Q2 Q1 out: G8 ;  
or: G9 in: G7 G8 out: J0 ;  
and: G10 in: Q2 Q1N out: G10 ;  
and: G11 in: Q2N Q1 out: G11 ;  
or: G12 in: RN G10 G11 out: K0 ;
```



Test Vectors

 - Unlike with combinational design, order of vectors now matters
- Think of the list of vectors (top to bottom) as you would a timing diagram (left to right)




- Ideally each transition will be tested
 - 90 vectors!

cR
00
10
01
11
01
11
01
11
01
11
01
11
01
11
01
11
01
11
01
11
00
10



Output

 - Unlike with combinational design, state of output can be unknown
 - Indicated by a '2' in the .out file
- Using the same vector file output of both circuits should be identical
- Let's take a look...




Basic Steps

 - 1) Describe the state machine based on the design spec
 - 3 different ways
- 2) Choose flip-flops
- 3) Create circuit excitation table
- 4) Construct K-maps for:
 - flip-flop inputs
 - primary outputs
- 5) Obtain minimized SOP equations
- 6) Draw logic diagram
- 7) Simulate to verify design & debug as needed
- 8) Perform circuit analysis & logic optimization**



Analysis & Optimization

- To minimize the area of the circuit:
 - Use the smallest number of memory elements
 - Minimize area of combinational logic
- For timing analysis
 - With less control over the flip-flop propagation delay focus on combinational logic
 - Path analysis from inputs to outputs
 - Inputs: flip-flop outputs (Q's), external inputs ®
 - Outputs: flip-flop inputs (J, K, D's), external outputs (not present in this example)
 - Consider each path...



Analysis & Optimization

- JK circuit

- $G=13$
- $G_{IO}=43$
- $G_{del}=2$
All paths
- $P_{del}=13$
R->K0

- D circuit

- $G=9$
- $G_{IO}=35$
- $G_{del}=2$
All paths
- $P_{del}=15$
R->All outputs

- JK is faster, D is smaller
- What effect do the flip-flops have?



Analysis & Optimization

- These circuits are not necessarily optimal
 - Make changes
 - Perform analysis again to show improvement
 - **Re-check** design (simulation)




Basic Steps

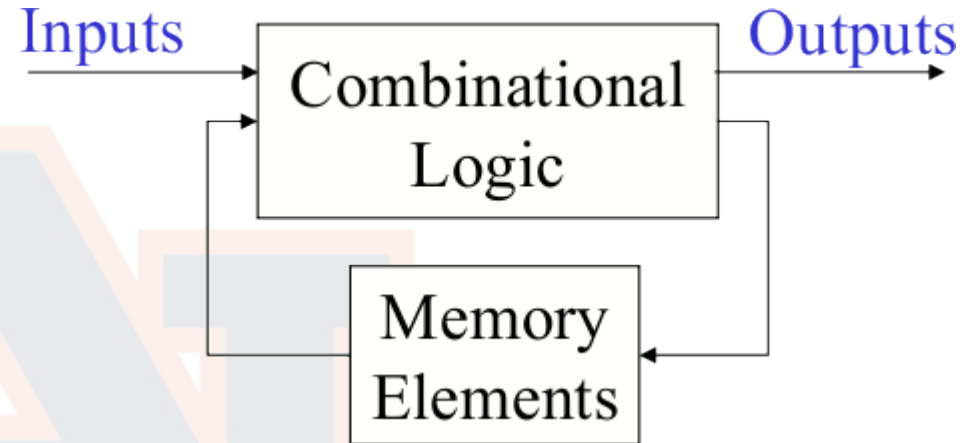- 1) Describe the state machine based on the design spec
- 3 different ways
- 2) Choose flip-flops
- 3) Create circuit excitation table
- 4) Construct K-maps for:
 - flip-flop inputs
 - primary outputs
- 5) Obtain minimized SOP equations
- 6) Draw logic diagram
- 7) Simulate to verify design & debug as needed
- 8) Perform circuit analysis & logic optimization**




Huffman: Mealy & Moore

- Outputs are not always the state of the machine directly
- Huffman Model divided into two sub-types
- Mealy Model
 - Outputs dependent on current state **and** inputs
- Moore Model
 - Outputs dependent on current state **only**




Huffman: Mealy & Moore

 - Outputs are not always the state of the machine directly
- Huffman Model divided into two sub-types
- Mealy Model
 - Outputs dependent on current state **and** inputs
- Moore Model
 - Outputs dependent on current state **only**



Huffman: Mealy & Moore

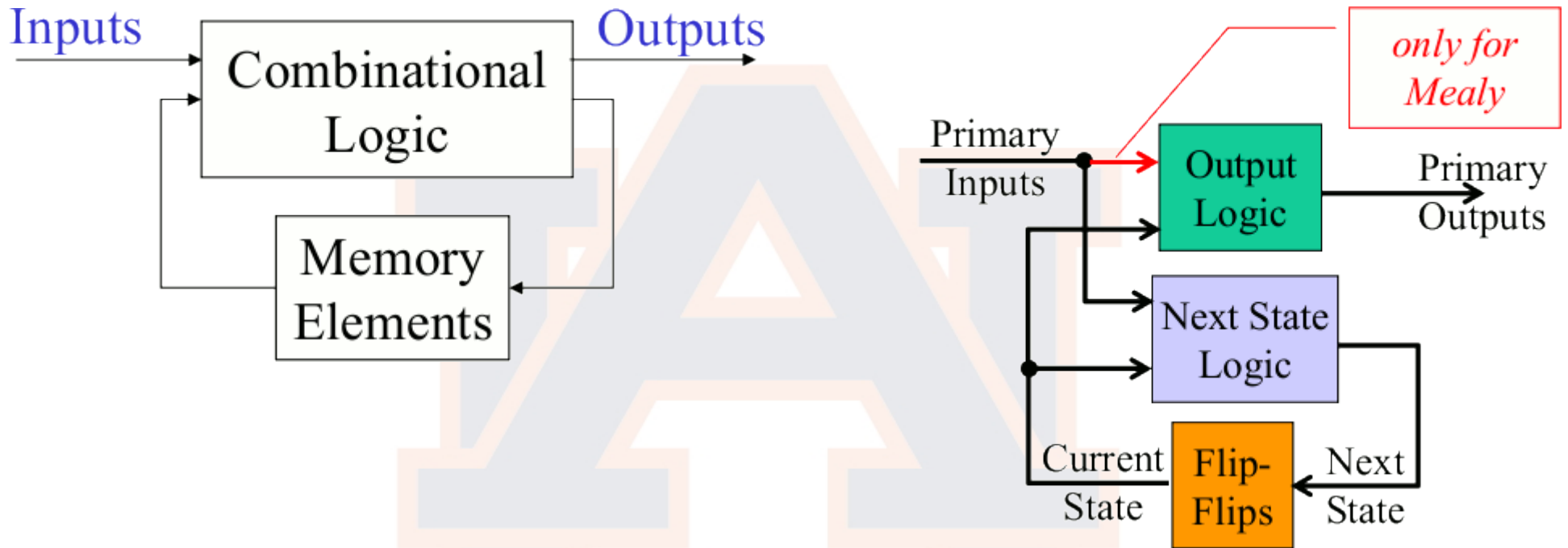

- More detail in Huffman model reveals difference
- Next state logic the same for Mealy and Moore. Only output logic differs



Mealy Example


| | | | | | |
|----|--|-----|----|----|----|
| | | X Y | | | |
| In | | 00 | 01 | 11 | 10 |
| 0 | | 0 | 1 | X | 0 |
| 1 | | 1 | 0 | X | 0 |

| | | | | | |
|----|--|-----|----|----|----|
| | | X Y | | | |
| In | | 00 | 01 | 11 | 10 |
| 0 | | 1 | 0 | X | 0 |
| 1 | | 0 | 0 | X | 1 |

$$D_X = In'Y + InX'Y' \quad D_Y = InX + In'X'Y'$$

Input / Output

State order XY

 

| Input | Curr. State | | Next State | | X | Y | Output |
|-------|-------------|---|------------|---|---|---|--------|
| In | X | Y | X | Y | D | D | |
| 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | X | X | X | X | X |

| | | | | | |
|----|--|-----|----|----|----|
| | | X Y | | | |
| In | | 00 | 01 | 11 | 10 |
| 0 | | 1 | 0 | X | 1 |
| 1 | | 1 | 1 | X | 0 |

$$O_{Mealy} = In'Y' + InX'$$




Moore Example

| | | X Y | | | |
|----|---|-----|----|----|----|
| In | | 00 | 01 | 11 | 10 |
| 0 | 0 | 0 | 1 | X | 0 |
| 1 | 1 | 1 | 0 | X | 0 |

| | | X Y | | | |
|----|---|-----|----|----|----|
| In | | 00 | 01 | 11 | 10 |
| 0 | 0 | 1 | 0 | X | 0 |
| 1 | 1 | 0 | 0 | X | 1 |

$$D_X = In'Y + InX'Y' \quad D_Y = InX + In'X'Y'$$

| Input | Curr. State | | Next State | | X | Y | Output |
|-------|-------------|---|------------|---|---|---|--------|
| In | X | Y | X | Y | D | D | |
| 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | X | X | X | X | X |

 

| | | X Y | | | |
|----|---|-----|----|----|----|
| In | | 00 | 01 | 11 | 10 |
| 0 | 0 | 1 | 0 | X | 0 |
| 1 | 1 | 1 | 0 | X | 0 |

$$O_{\text{Moore}} = X'Y'$$




Mealy & Moore Circuits

$$O_{\text{Mealy}} = \text{In}'Y' + \text{In}X'$$

$$D_X = \text{In}'Y + \text{In}X'Y'$$

$$D_Y = \text{In}X + \text{In}'X'Y'$$

$$O_{\text{Moore}} = X'Y'$$

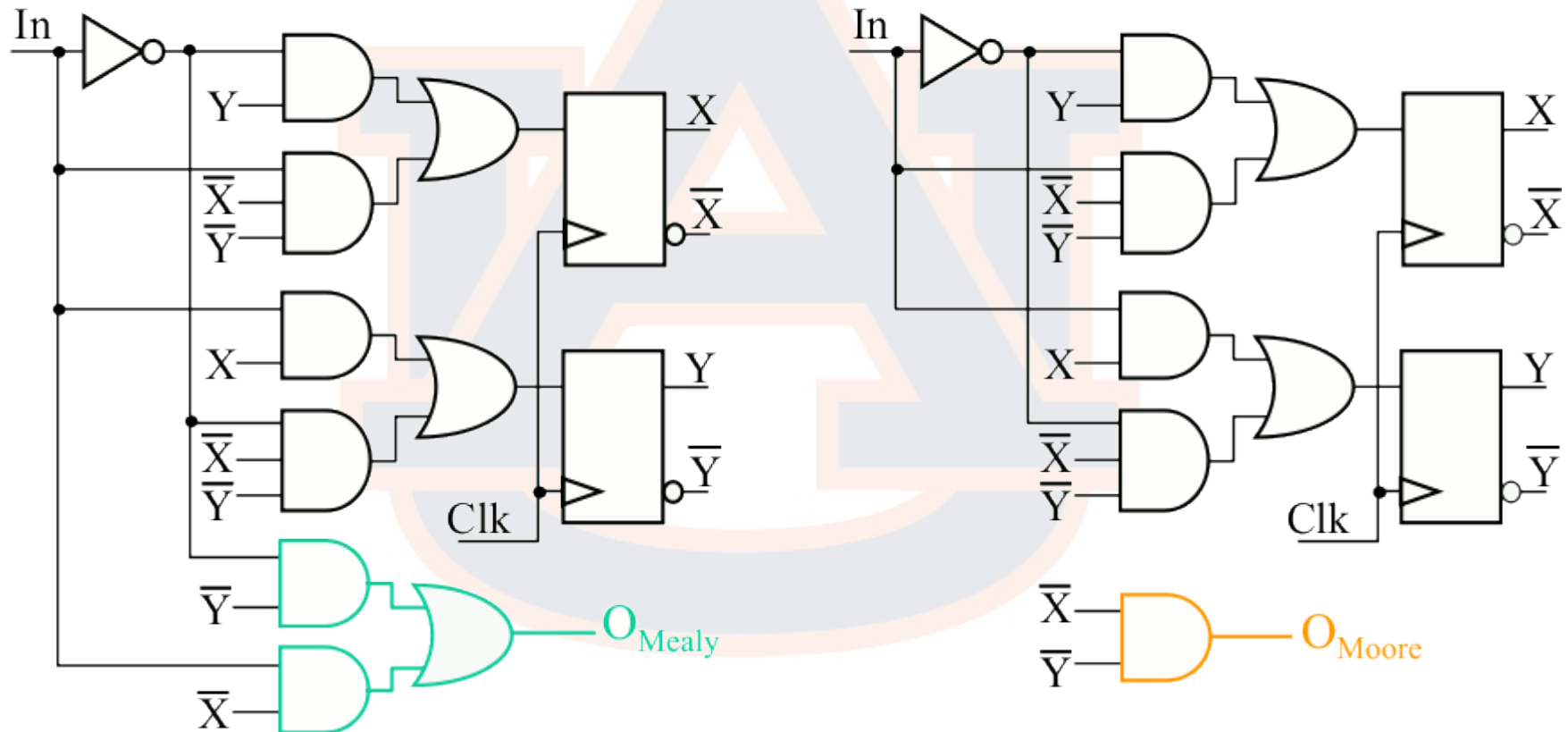

- Note: Similarity in next state logic, difference in output




Mealy/Moore Summary

- Mealy
 - Outputs dependent on current state **and** inputs
 - More flexible model, can result in fewer states
 - Care must be taken not to transition inputs near time to read outputs
- Moore
 - Outputs dependent on current state **only**
 - Less flexible model, may require more states
 - Output only changes on clock, easier to time reads of outputs




 
Example

- Design a synchronous circuit that will count from 0 to 15 by 3's and then rollover to 0. Output should change on the positive edge of the clock.




State Diagram/Flip-Flops

 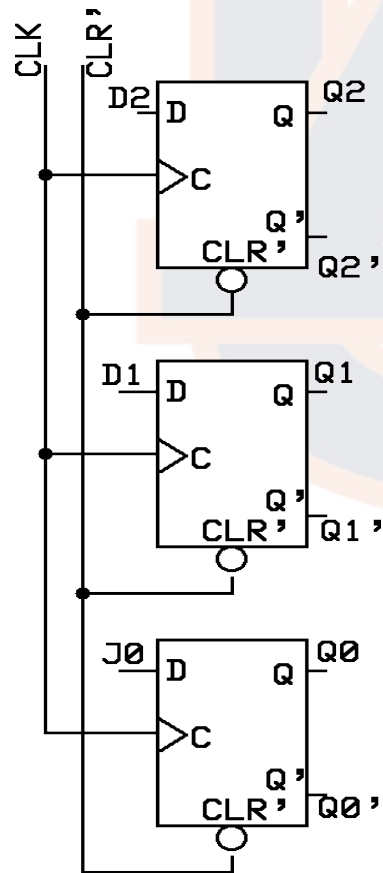- Could use state to represent output directly (4 FFs)
- With only six states 3 bits could represent state with smaller circuit (3 FFs)




State Diagram/ Outputs

 - Using a Moore model, a 3 bit value is assigned to each state
- Output of each state is not changed
- Additional expressions needed to convert from state to output



Excitation Table

 - Table indicates order of states **and** output for each current state



| Curr. State | | | Next State | | | Excitation | | | Output | | | |
|-------------|----|----|------------|----|----|------------|----|----|--------|----|----|----|
| Q2 | Q1 | Q0 | Q2 | Q1 | Q0 | D2 | D1 | D0 | c3 | c2 | c1 | c0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |



Next State K-maps

- [FF Inputs]=f(Current State, External Inputs)

| Curr. State | | | Next State | | | Excitation | | | Output | | | |
|-------------|----|----|------------|----|----|------------|----|----|--------|----|----|----|
| Q2 | Q1 | Q0 | Q2 | Q1 | Q0 | D2 | D1 | D0 | c3 | c2 | c1 | c0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |

| Q2\Q1, | D2 | | | | Q2\Q1, | D1 | | | | Q2\Q1, | D0 | | | |
|--------|----|----|----|----|--------|----|----|----|----|--------|----|----|----|----|
| Q0 | 00 | 01 | 11 | 10 | Q0 | 00 | 01 | 11 | 10 | Q0 | 00 | 01 | 11 | 10 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | X | X | 1 | 0 | 0 | X | X | 1 | 1 | 0 | X | X |

$D2 = Q2 \cdot \overline{Q0} + Q1 \cdot Q0$

$D1 = \overline{Q2} \cdot \overline{Q1} \cdot Q0 + Q1 \cdot \overline{Q0}$

$D0 = \overline{Q0}$



Output K-maps

- [Outputs]=f(Current State)

| Curr. State | | | Next State | | | Excitation | | | Output | | | |
|-------------|----|----|------------|----|----|------------|----|----|--------|----|----|----|
| Q2 | Q1 | Q0 | Q2 | Q1 | Q0 | D2 | D1 | D0 | c3 | c2 | c1 | c0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |

| Q2\Q1, | | c3 | | | | Q2\Q1, | | c2 | | | |
|--------|---|----|----|----|----|--------|---|----|----|----|----|
| Q0 | | 00 | 01 | 11 | 10 | Q0 | | 00 | 01 | 11 | 10 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | X | X | 1 | 1 | 1 | X | X | |

$$c3 = Q2 + Q1 \cdot Q0$$

$$c2 = Q2 + Q1 \cdot \overline{Q0}$$


| Q2\Q1, | | c1 | | | | Q2\Q1, | | c0 | | | |
|--------|---|----|----|----|----|--------|---|----|----|----|----|
| Q0 | | 00 | 01 | 11 | 10 | Q0 | | 00 | 01 | 11 | 10 |
| 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | |
| 1 | 0 | 0 | 1 | X | X | 1 | 0 | 1 | X | X | |

$$c1 = \overline{Q1} \cdot Q0 + Q1 \cdot \overline{Q0}$$

$$c0 = Q0$$



Schematic

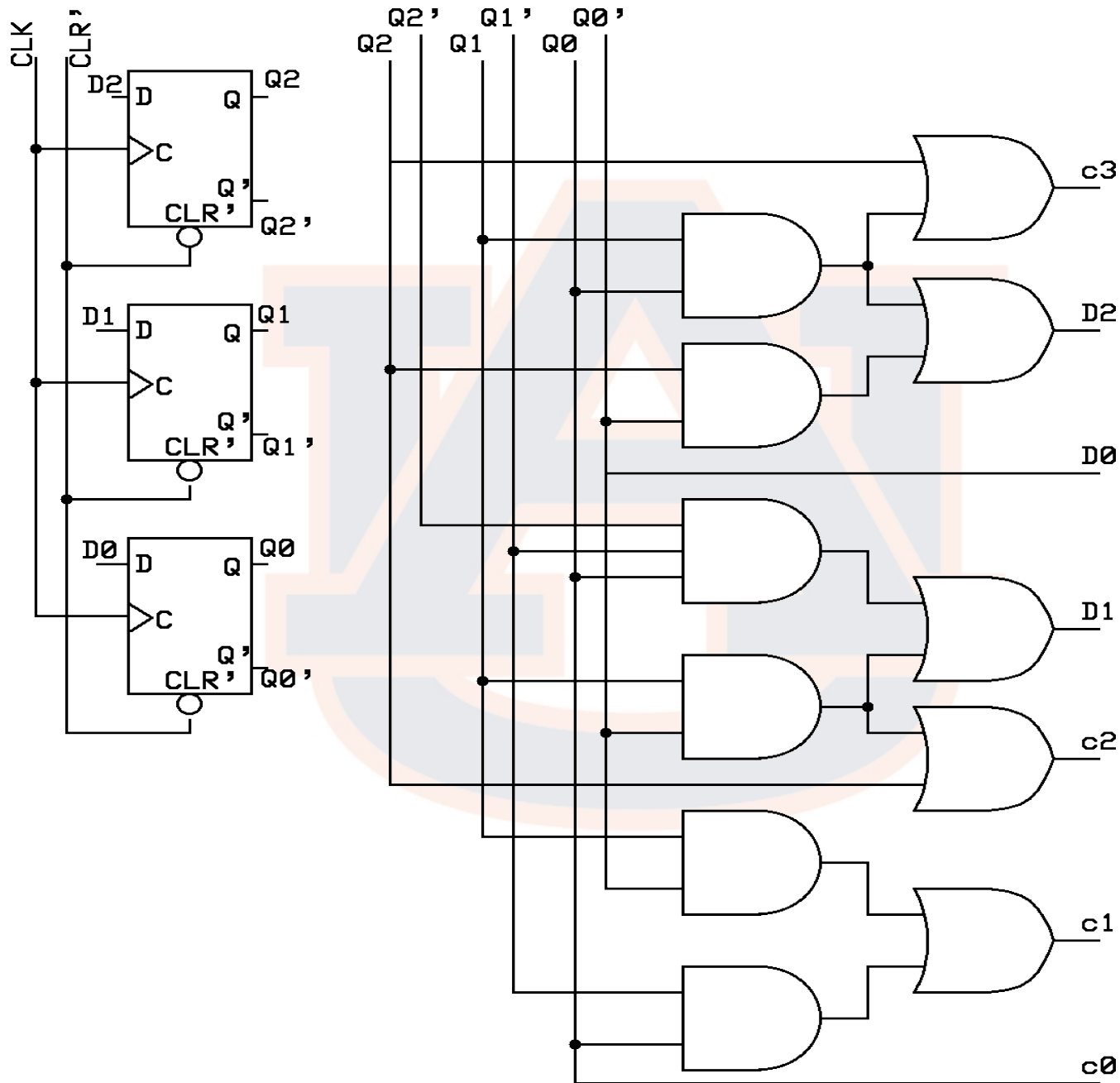

Keypad Example

Design a sequential circuit to recognize a three digit combination entered on a keypad. The keypad has four buttons labeled 0 through 3. When a key is pressed the binary value of the key is available as the two bit number, $b_1 b_0$. Once b_1 and b_0 are stable, a clock pulse will occur (clk). The combination to open the lock will be 213_{10} .

